



# Spin it to Light it



*How light bulbs with different voltage need different energy levels for it to light the brightest*

By Lana Z, Gr.5

# Hypothesis

---



If the light bulb has **higher voltage**, then it would require **more force and speed** because we need **more electricity** to light up the light bulb.



# Research



⚡ **Electricity** is energy that is used to power up homes and cities.

⚡ To light a light bulb, there must be a **closed circuit**.

⚡ A closed circuit needs to have an **electricity supply, conductors** and a **light bulb**.

⚡ The light bulb will tell you if the circuit is **closed or not**.

⚡ There are two **types of circuits**: series circuit and parallel circuit.


⚡ In my experiment, I used a **dynamo with a hand cranker** as my electricity supply instead of a battery.

⚡ When you spin the hand cranker, the magnet in the dynamo will rotate which creates kinetic energy. Using the **properties of electromagnetism**, it will convert the **kinetic energy into electrical energy**, also known as electricity, which will flow through the **copper wires** and **light up** the light bulb.
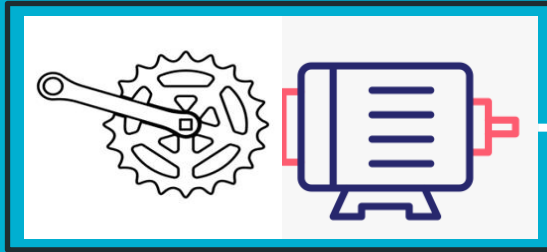
# Circuit diagram

Using properties of electromagnetism converts kinetic energy to electricity


Kinetic energy when you spin the hand cranker



Hand cranker

Dynamo

Electricity flows through copper wires

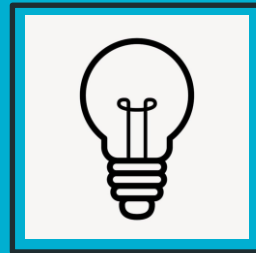

Light bulb

Copper wires

Dynamo with hand cranker  
and with two terminals



Voltmeter with  
positive and  
negative terminals



3 light bulbs  
with different  
voltage but the  
same ampere

## Materials needed



4 copper wires



Lamp socket  
with two  
terminals

# Variables

---



Copper wires



Dynamo with hand cranker




Voltmeter



Light bulbs with different voltage



Speed and force

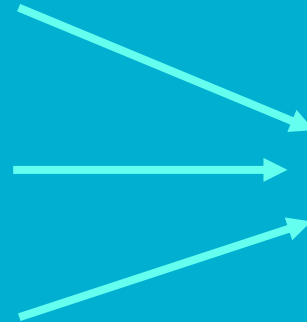

Controlled variables



Responsive variable



Manipulative variables



# Procedures (1 / 4)


## Preparing the circuit

1. Connect the red terminal of the dynamo to the positive terminal of the voltmeter using one copper wire
2. Connect the black terminal of the dynamo to the negative terminal of the voltmeter using one copper wire
3. Connect one terminal of the dynamo to one terminal of the lamp socket using one copper wire
4. Connect the other terminal of the dynamo to the other terminal of the lamp socket using one copper wire

Note: There are two wires on each terminal of the dynamo. This will create a parallel circuit

5. Add Light Bulb C to the lamp socket. Twist the light bulb until it tightens and the bottom touches the metal plate

This is what the circuit looks like

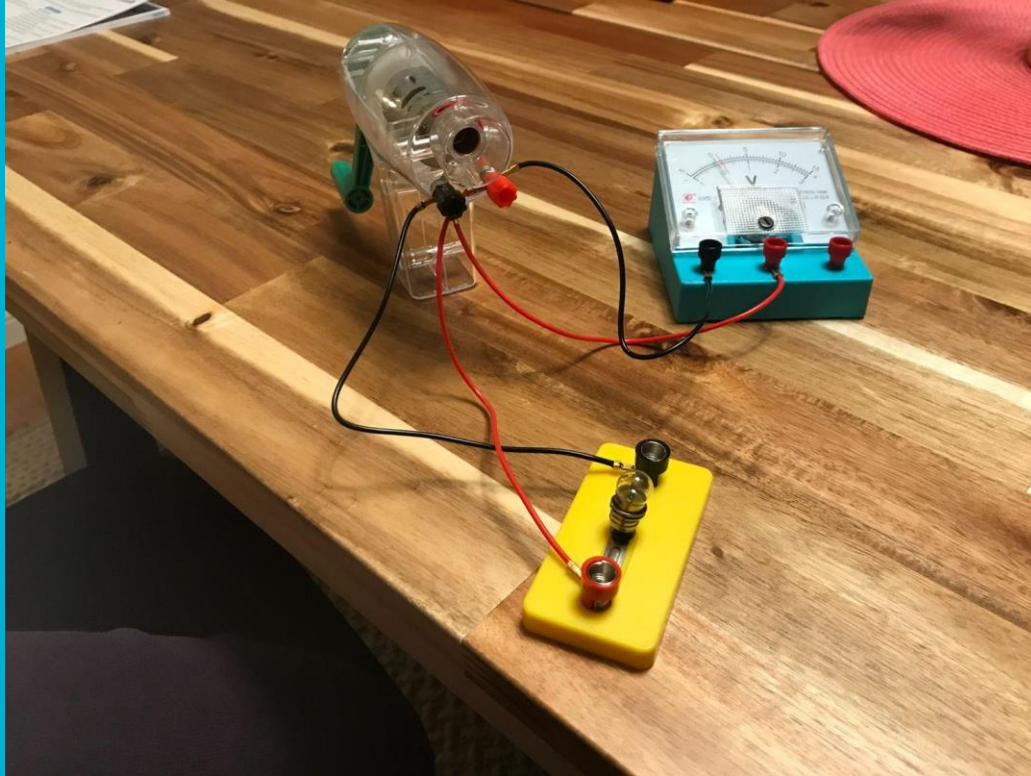





# Procedures (2 / 4)

## 2

### Experiment

1. Spin the hand cranker that is on the dynamo in a clockwise direction
2. Spin the hand cranker until the voltmeter reads 1 volt
3. Observe the brightness of the light bulb and record your observations
4. Spin the hand cranker faster until the voltmeter reads 2 volts
5. Observe the brightness of light bulb and record your observation
6. Spin the hand cranker even faster until the voltmeter reads 3 volts
7. Observe the brightness of the light bulb and record your observations
8. Repeat the steps above with Light Bulb B then Light Bulb A



# Procedures (3 and 4 / 4)

3

## Analyse

Perform your analysis by comparing your observations on the brightness of Light Bulb A, B and C

4

## Conclude

Form your conclusion



# Observations for Light Bulb C

Spin faster

Spin even faster



Light bulb	Voltage	Reading on the voltmeter		
		1 volt	2 volts	3 volts
C	2.5V	Dim	Bright	Very bright
C	2.5V	Dim	Bright	Very bright
C	2.5V	Dim	Bright	Very bright
C	2.5V	Dim	Bright	Very bright
C	2.5V	Dim	Bright	Very bright



# Observations for Light Bulb B

Spin faster

Spin even faster



Light bulb	Voltage	Reading on the voltmeter		
		1 volt	2 volts	3 volts
B	3.8V	Very dim	Dim	Bright but not as bright as Light Bulb C
B	3.8V	Very dim	Dim	Bright but not as bright as Light Bulb C
B	3.8V	Very dim	Dim	Bright but not as bright as Light Bulb C
B	3.8V	Very dim	Dim	Bright but not as bright as Light Bulb C
B	3.8V	Very dim	Dim	Bright but not as bright as Light Bulb C



# Observations for Light Bulb A

Spin faster

Spin even faster



Light bulb	Voltage	Reading on the voltmeter		
		1 volt	2 volts	3 volts
A	6.3V	Very dim, Almost no light	Very dim	Dim
A	6.3V	Very dim, Almost no light	Very dim	Dim
A	6.3V	Very dim, Almost no light	Very dim	Dim
A	6.3V	Very dim, Almost no light	Very dim	Dim
A	6.3V	Very dim, Almost no light	Very dim	Dim



# Overall Observations

Each light bulb gave the same results for all five attempts

Spin faster



Spin even faster



Light bulbs	Voltage	Reading on the voltmeter		
		1 volt	2 volts	3 volts
C	2.5V	Dim	Bright	Very bright
B	3.8V	Very dim	Dim	Bright but not as bright as Light Bulb C
A	6.3V	Very dim, Almost no light	Very dim	Dim

# Analysis

---



In order to get a higher voltage, I need to spin the hand cranker faster



When I spun the hand cranker until the reading on the voltmeter said 3 volts, Light Bulb B was not as bright as Light Bulb C because Light Bulb B is with a higher voltage compared to Light Bulb C (3.8V vs 2.5V) and 3 volts is not enough for Light Bulb B to light up the brightest because it requires 3.8V for that



At 3 volts, Light Bulb A was the least bright because it requires the highest voltage (6.3V vs 3.8V vs 2.5V) to light the brightest



Even if there is not enough voltage flowing, a light bulb can still light up, but it will not be at its brightest just like Light Bulb C

# Sources of Error

---



When the circuit is not closed. Could be because of:



Wires are not connected properly



Light Bulb is burned out



The motor might not be working



# Conclusion

---




The **higher the voltage** of the bulb is, the **faster** I need to spin the hand cranker using **more energy** so that there is **enough electricity flow** to light up the light bulb the brightest.
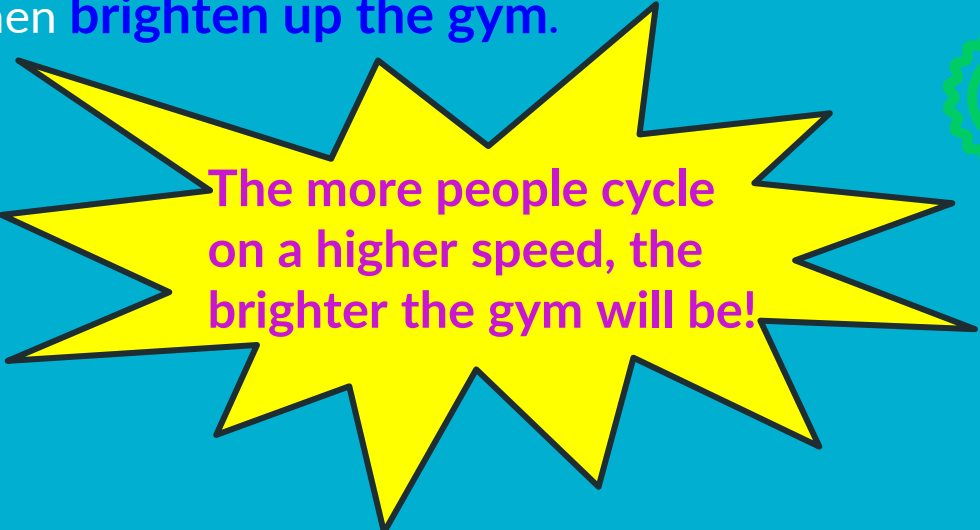
# Concept Application

---

In a **bike spinning gym**, we can apply this concept as an **alternative source** of electricity to light the gym up by having light bulbs on the bikes. **When someone cycles on the bike** it will light the light bulb up using **kinetic energy** which will then **brighten up the gym**.



The more people cycle on a higher speed, the brighter the gym will be!



## BENEFITS

- ★ Save on electricity bills
- ★ Cheaper membership fees
- ★ Attracts more people to the gym

# Current Applications

---

In a **hydropower plant**, when the moving water hits the turbine, similar to the dynamo concept, it will create electricity enough to light up a city.



**Light on a bicycle** where the light will light up as the cyclist cycles




Dynamo-operated  
handheld **flashlights**



# Citations

---

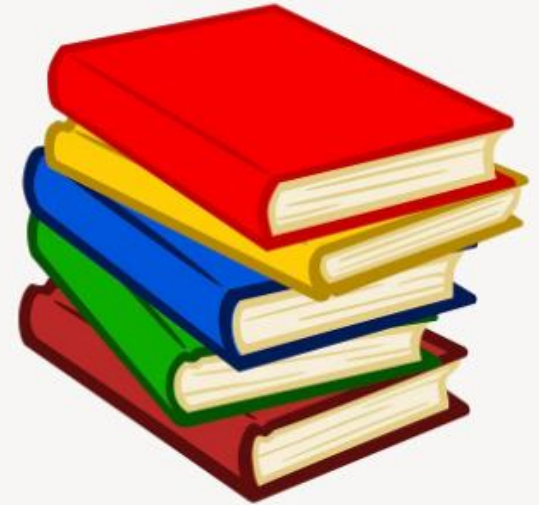1. Khan Academy <https://www.khanacademy.org/>
2. Britannica Kids <https://kids.britannica.com/>
3. Twinkl <https://www.twinkl.ca/>
4. Study.com <https://study.com/>
5. BYJU'S <https://byjus.com/>
6. U.S Energy Information Administration  
<https://www.eia.gov/>
7. JLab <https://education.jlab.org/>
8. Quizlet <https://quizlet.com/gb>
9. A True Book™ - Physical Science: Electricity and Magnetism By Cody Crane





# Acknowledgement

- ★ I thank my **mom and dad** for helping and supporting me through my science fair challenges
- ★ I would also thank **Ms.Tang** for giving me guidance and feedback to complete my science fair project
- ★ Thank you to my homeroom teacher, **Mr.Chris** who introduced me to electricity circuits which I then developed further by using dynamos in the circuit



**Thank you!**